

Paper Id: **130103**

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

B TECH
(SEM –I) THEORY EXAMINATION 2019-20
Electronics Engineering


Time: 3 Hours**Total Marks: 100****Note: 1. Attempt all Sections. If require any missing data; then choose suitably.****SECTION A****1. Attempt all questions in brief.****2 x 10 = 20**

a.	Differentiate between Clipper and Clamper circuit.
b.	What you mean by Doping. Describe its need.
c.	Give all the Equivalent /Approximation circuits of a Diode.
d.	Why the Q-point varies in transistors.
e.	Differentiate between N-type and P-type semiconductor.
f.	Define Threshold Voltage for an E-MOSFET. Also define I_{DSS} for an JFET.
g.	Describe trans conductance curve of JFET.
h.	Explain the use of Digital multimeter.
i.	Explain the form factor of full wave rectifier.
j.	Explain the effect of temperature on reverse saturation current.

SECTION B**2. Attempt any THREE of the following:****10 x 3 = 30**

a.	Write the diode current equation of a p-n junction and explain the V-I characteristics from it.?
b.	With the help of block diagram explain the working of digital voltmeter.
c.	Explain half wave rectifier and also drive its avg. and rms. current value
d.	Describe the working of voltage multiplier circuit.
e.	Explain the construction and working of E - MOSFET

SECTION C**3. Attempt any one part of the following:****10 x 1 = 10**

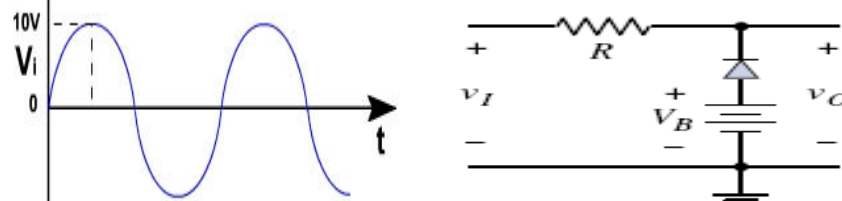(a)	Differentiates between the Avalanche breakdown and Zener breakdown
(b)	Draw the output waveform for the circuit for the circuit of Fig. 

4. Attempt any one part of the following:**10 x 1 = 10**

(a)	Calculate Q point for a Voltage Divider Biased CE amplifier having $R_1=10K\Omega$, $R_2=5K\Omega$, $R_C=1K\Omega$, $R_E=500\Omega$, $V_{CC}=10V$, $\beta=100$.
(b)	Explain the construction and working principle of NPN transistor.

Paper Id: **130103**

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

5. Attempt any *one* part of the following:

10 x 1 = 10

(a)	Explain the construction, operation and characteristics of N channel JFET
(b)	Draw and Explain the working of:-(1) Integrator using OP-AMP, (2) Summing amplifier using OP-AMP

6. Attempt any *one* part of the following:

10 x 1 = 10

(a)	Explain the various number system and its conversion of bases (decimal, binary, octal and hexadecimal numbers)
(b)	Minimize using K-map and realize using NAND gates only. $F(A, B, C, D) = \sum m(3, 4, 5, 7, 9, 13, 14, 15)$. $d(0, 2, 8)$

7. Attempt any *one* part of the following:

10 x 1 = 10

(a)	Describe measurement of Voltage, Frequency & Phase using CRO
(b)	Describe the working of Digital Multimeter with their block diagram.